

MOSFET-based Joule Thief steps up voltage

[sajjad Haidar](#) - February 23, 2015

A simple blocking oscillator circuit can be used to step up voltage using properties of coil inductance ($V = L di/dt$). Such a circuit is shown in **Figure 1**, which is more commonly called a [Joule thief](#).

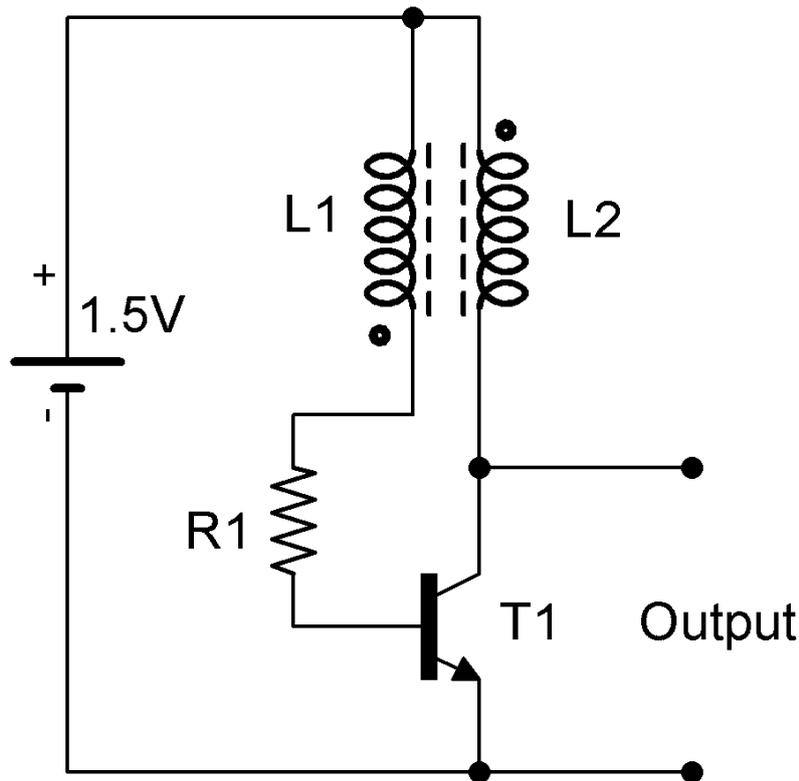


Figure 1 Basic Joule Thief circuit

The output will be pulses of voltage that can be filtered using a diode and capacitor. As there is no regulation, the output voltage will vary with the input voltage or load. As this circuit uses a BJT, the supply voltage needs to be at least 0.7V to work, and with enhancement-mode MOSFETs, the supply voltage must usually be even higher.

In this Design Idea, a low-threshold MOSFET (Q1) is used with coupled coils L1 and L2 to act as a Joule thief circuit.


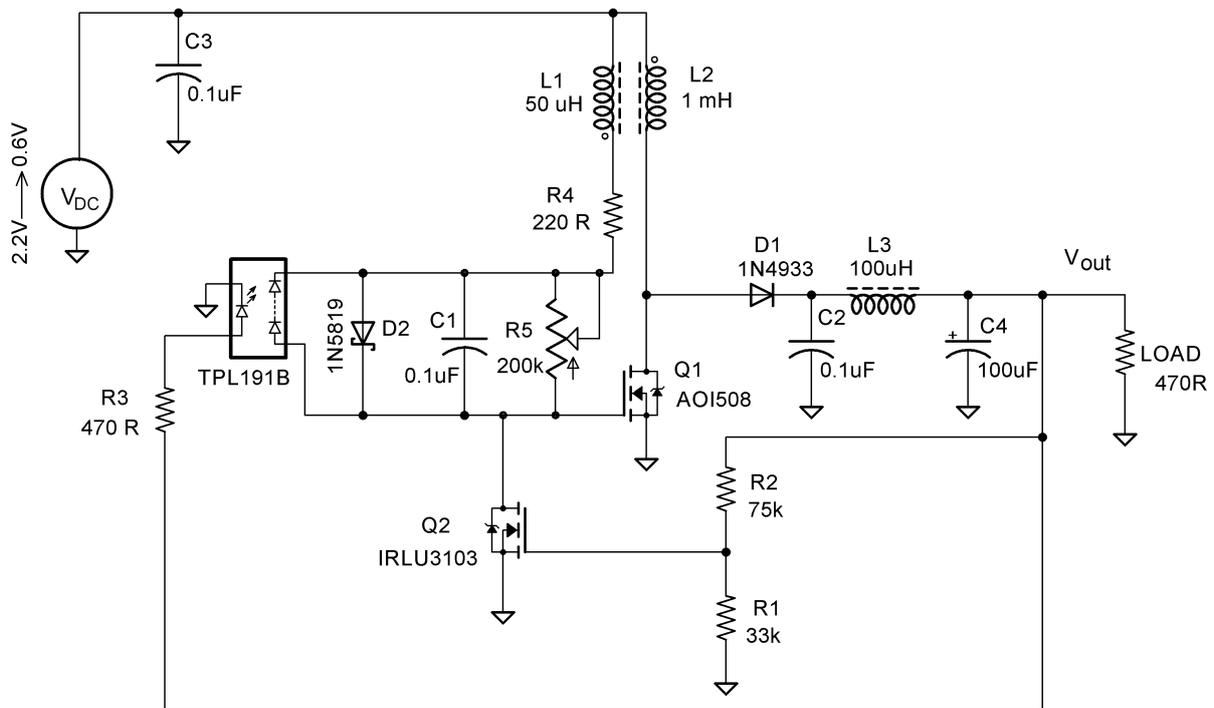


Figure 2 MOSFET-based Joule Thief

A toroidal ferrite core is used to make the coupled coil or transformer. A photovoltaic optocoupler, [TLP191B](#), is used to circumvent the problem with the threshold voltage. Part of the output is used to power TLP191B to make an isolated voltage source in series with the gate of Q1 ([AOI508](#)). This isolated voltage can be controlled by the pot R5; capacitor C1 is used to pass the pulses produced by L1 to the gate for switching.

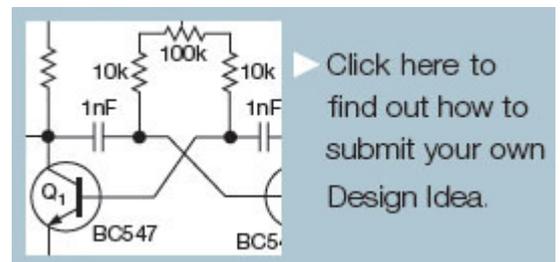

For regulation, another MOSFET, Q2 ([IRLU3103](#)), is used. The threshold voltage of Q2 is used to regulate the output voltage. When the output reaches 5V, the divider formed by R1 and R2 makes Q2 conduct, and the oscillation ceases, causing the output voltage to drop. As the threshold voltage is not very sharp, the regulation is not usually that good.

To start working, the circuit initially needs higher voltage than the V_{th} of Q1. At 1.9V, the circuit oscillates, and the output voltage is 5.1V. As the input voltage goes down, the oscillator stops at 1.4V. By adjusting pot R5 to higher values, the minimum operating voltage can go as low as 0.6V. The input-output voltages are shown graphically in **Figure 3**.

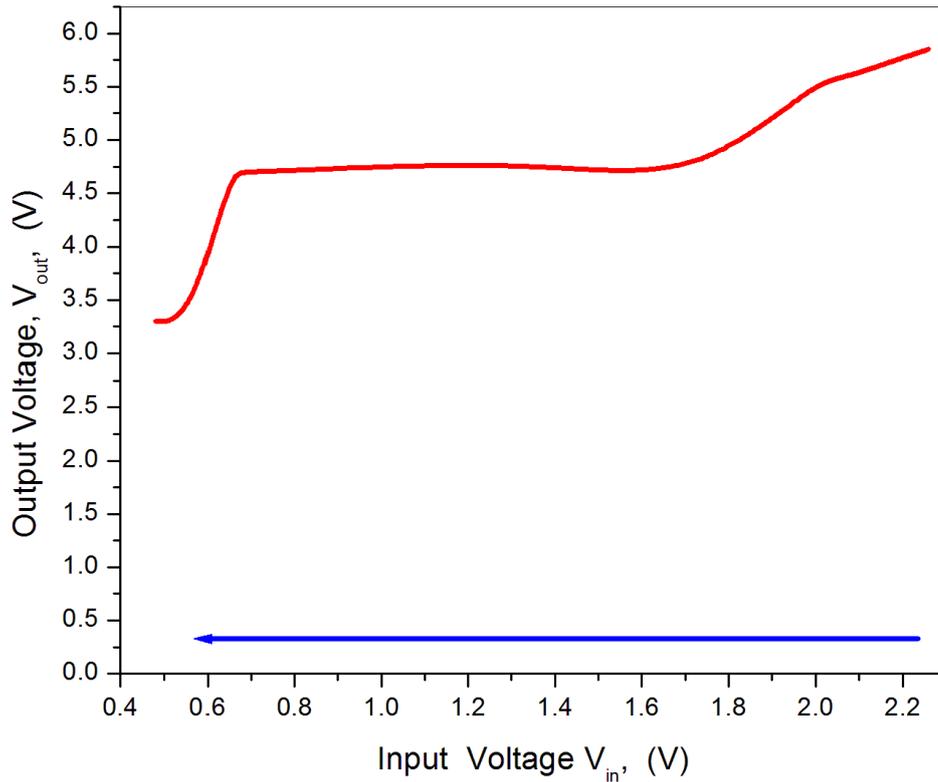


Figure 3 V_{in} vs. V_{out}

Efficiency drops at lower input voltages. The efficiency for $V_{in} = 2.5V$ is 48% and goes down to 36% at 0.6V.

In my application, the circuit is connected to a supercapacitor of 150F @ 2.5V, which is charged up to 2.3V. The charged capacitor powers the load (4700) for 38 minutes, until its voltage reaches 0.6V. The implemented circuit with the supercapacitor connected is shown in **Figure 4**.

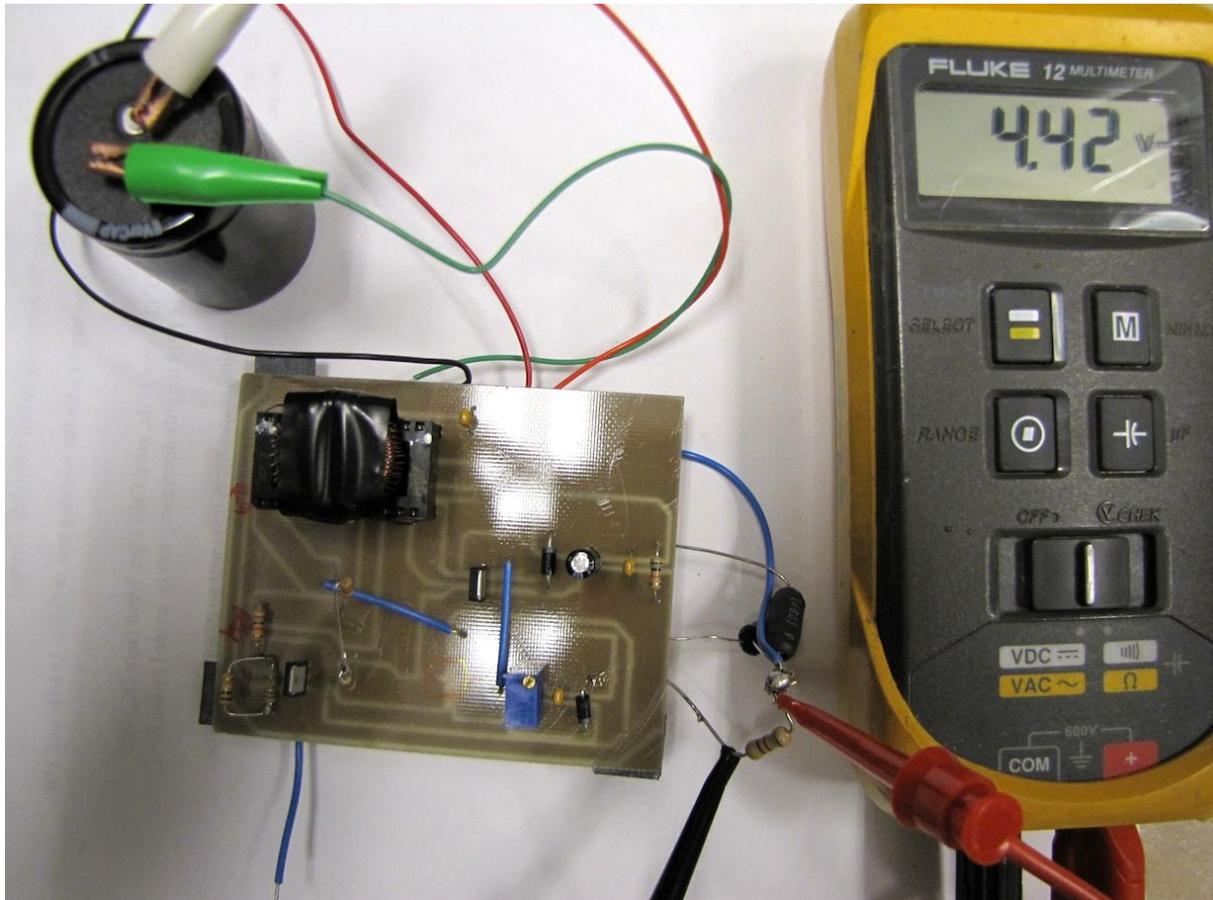


Figure 4 The built circuit

Note: In “[Low Voltage Driven Oscillator Circuit](#)”, a circuit is shown with a JFET or depletion-mode MOSFET, which will work as a DC to DC converter with an input voltage as low as 0.1V. Simulation results show that its efficiency is very poor. Most of the power will be wasted by the FET and the source resistance.

READ MORE
designideas

Also see:

- [JFET-based dc/dc converter operates from 300-mV supply](#)
- [Self-oscillating H bridge lights white LED from one cell](#)
- [Pocket white-LED torch is power efficient](#)
- [LED-flashlight circuit works at voltages as low as 0.5V](#)