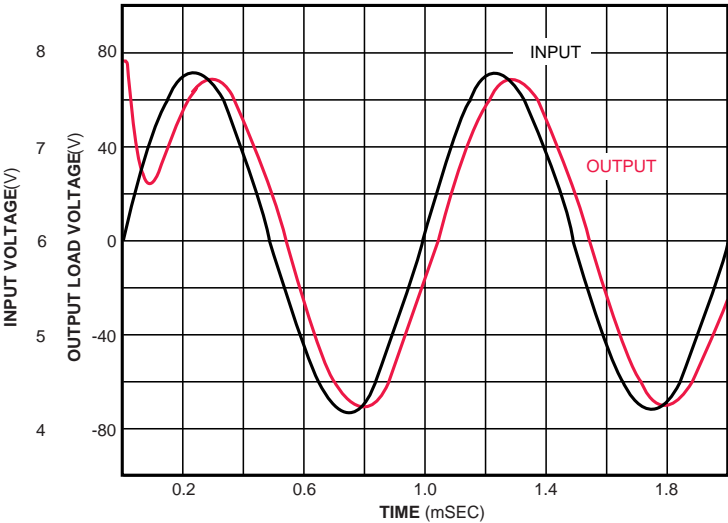


Figure 7



Ignoring the feedback circuitry of X3 and X4, a 1-kHz, 3.5V p-p sine wave with offset at V_{in} produces a 120V p-p sine wave across the load. drift.