

**Circuits provide 4- to 20-mA PWM control  
Figure 2**

**This simplified version of the circuit in Figure 1 has a  
synchronization input instead of an output.**