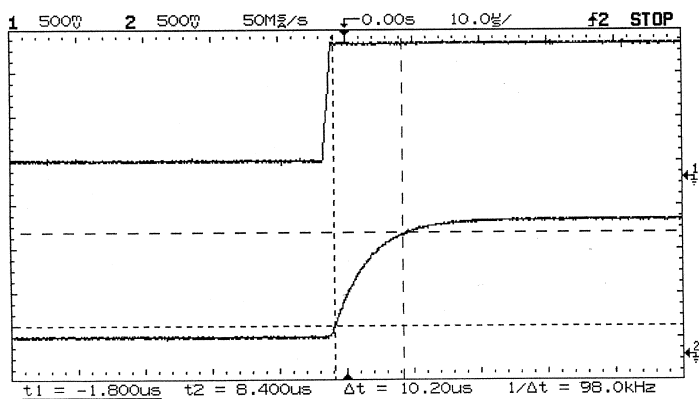


Circuit uses simple LED for near-IR light Figure 2



IC₂ in Figure 1 delivers a clean response to a modulation-input step function.