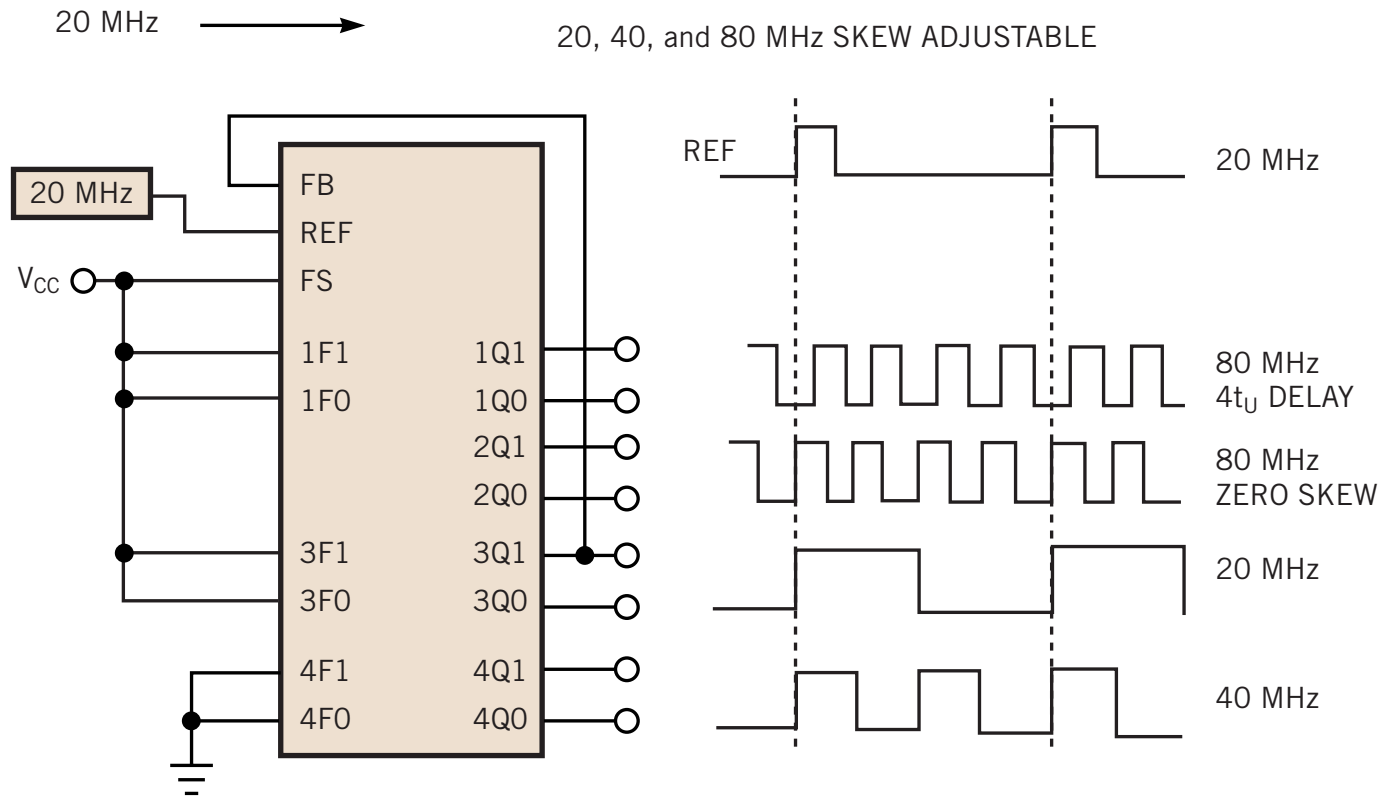


**Figure 4**



**Operating as a multifunction clock driver, a programmable-skew clock driver can generate 20-, 40-, and 80-MHz skew-adjustable outputs from one 20-MHz input.**