


WITH HOT-SWAP AND LOAD-SHARE POWER-MANAGER ICs,  
YOU CAN FORGET ABOUT SUPPLIES AND CONCENTRATE ON  
IMPORTANT SYSTEM CONSIDERATIONS.

# Hot-swap, load-share ICs protect circuits and supplies

IN SYSTEMS THAT USE multiple power supplies, hot swapping and current sharing are important considerations. Hot swapping refers to the insertion or removal of modules, boards, or power supplies into or from powered-up buses or connectors. PCMCIA, Universal Serial Bus (USB), CompactPCI, SCSI, and other standards provide strict mandates on inrush current, power-supply sequencing, and other power-up and -down aspects. Current, or load sharing involves equalizing, insofar as possible, the currents from multiple power supplies connected in parallel.

Several recent ICs provide hot-swapping and current-sharing management functions, eliminating the need to design discrete circuitry for protection and power integrity in your system.

Hot swapping can be a scary proposition (**Reference 1**). For example, if you insert a circuit board into a live backplane, the board's large bypass capacitors can draw inrush currents as large as 100A from the backplane's power bus. Unrestricted, these currents can destroy the board's bypass capacitors, metal traces, or even its connector pins. The inrush currents also produce a droop in the supply voltage to the rest

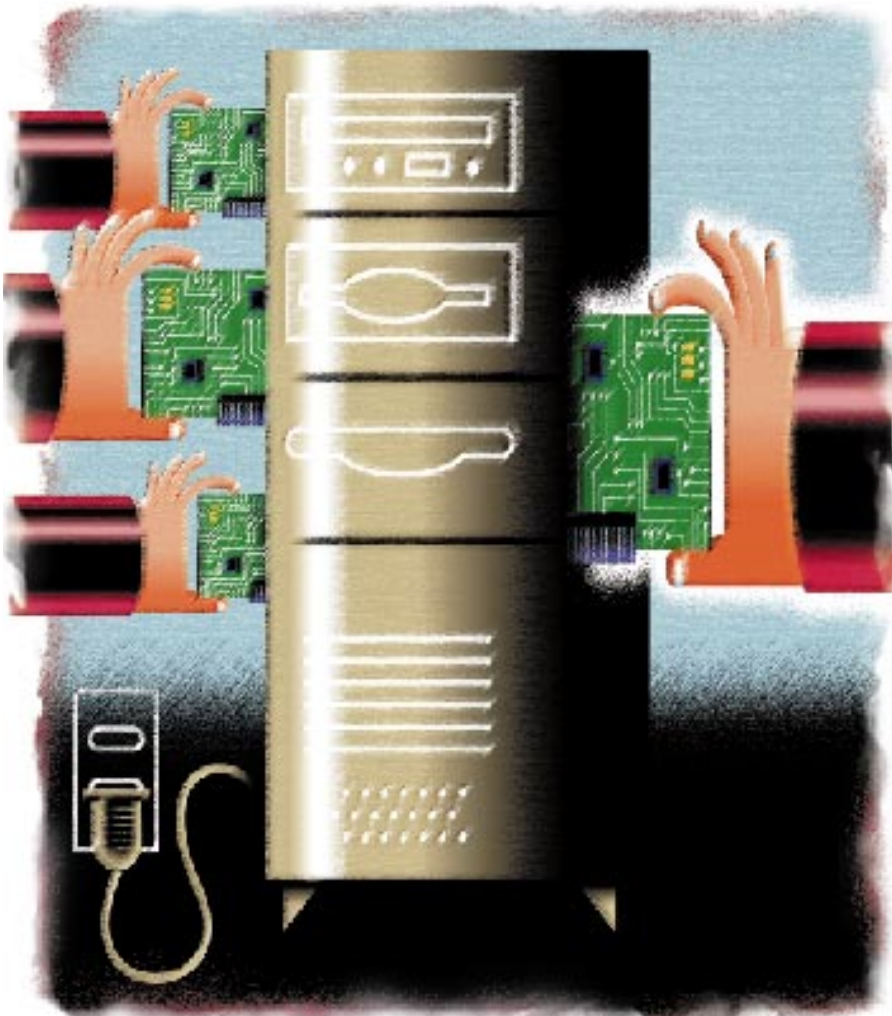

|  |     |
|--|-----|
| At a glance .....  | 114 |
| Current sharing<br>enhances performance<br>and fault tolerance ..... | 116 |
| For more<br>information.....   | 118 |

**AT A GLANCE**

- ▶ Excessive inrush currents or improper supply sequencing can zap delicate circuitry.

---

- ▶ Designing your own hot-swap protection steals time and effort from the meaty design challenges in your system.

---

- ▶ Live-insertion/removal capability in standards such as Universal Serial Bus and CompactPCI is not a luxury; it's a necessity.

---

- ▶ Equitable current sharing in multiple-supply systems minimizes thermal, stability, and reliability compromises.

of the circuit boards, which are connected to the backplane. The resulting out-of-regulation supply voltage can cause the affected boards to reset.

Most multiple-supply systems require the supply voltages to power up in a specific sequence. The sequence reverses upon power-down, with one supply kept alive long enough for software to control the power-down routine. Hot-swap power-management ICs provide both inrush protection and user-programmable supply sequencing. They also protect systems against power faults, and they monitor and signal the status of supply voltages and currents.

You can provide adequate hot-swap control, with perhaps a 90% success rate, by configuring controlled-turn-on FETs. RC-network delays at the gates of the FETs can produce the desired power-up delays. However, this approach has two potential problems: One is the long hours of tweaking that discrete analog circuits require. Although these hours may be enjoyable for some and relatively short for analog veterans, they are hours better spent on more mission-critical problems. The other problem is that 10% of the time, the solution doesn't work (Reference 1).

**APPLICATION SPECIFICITY**

Many hot-swap power-management ICs serve general-pur-

**TABLE 1—UNITRODE HOT-SWAP POWER-MANAGER ICs**

| Devices with internal pass MOSFET |                   |                     |                         |
|-----------------------------------|-------------------|---------------------|-------------------------|
| Device                            | Voltage range (V) | Maximum current (A) | R <sub>DS(ON)</sub> (Ω) |
| UCC3912                           | 3 to 8            | 4                   | 0.15                    |
| UCC3915                           | 7 to 15           | 5                   | 0.15                    |
| UCC3916                           | SCSI, 2, 3        | 2                   | 0.22                    |
| UCC3918                           | 3 to 6            | 5                   | 0.075                   |
| UCC3920                           | -3 to -15         | 4                   | 0.1                     |
| Devices with external pass MOSFET |                   |                     |                         |
| Device                            | Voltage range     |                     |                         |
| UCC1914                           | 4.5 to 35         |                     |                         |
| UCC3917                           | 7 to >1000        |                     |                         |
| UCC3919                           | 3 to 8            |                     |                         |
| UCC3913                           | -7 to >-1000      |                     |                         |
| UCC3921                           | -3 to >-1000      |                     |                         |


pose applications; others are application-specific. Application-specific devices target specific buses or standards, such as USB, CompactPCI, or the various flavors of SCSI. They handle the voltage and current levels that the given standard mandates, and they provide norm-specified protection, timing, and sequencing features. Unitrode Corp offers a broad spectrum of hot-swap managers (Table 1).

Most of the hot-swap managers in Table 1 are general-purpose devices; you choose your device according to the voltage and current requirements of the load. You can use the other devices in a variety of applications, but they are particularly useful in certain systems. The \$2.95 (1000)

UCC3915, for example, is intended for 12V hot-plugging applications, such as redundant array of independent disks (RAID) and popular communications ports, such as Ethernet and the advanced universal interface. Similarly, the \$2.95 (1000) UCC3920 serves communications ports that use -12V rails. The UCC3916 targets SCSI Termpower systems and offers SCSI, SCSI-2, and SCSI-3 compliance.

Figure 1 shows the circuit architecture of the UCC3920. The other Unitrode hot-swap managers with internal pass MOSFETs have similar topologies with individual variations. The 3-bit DAC in the UCC3920 lets you program the fault-level trip current using a 3-bit digital code. The


**Figure 1**

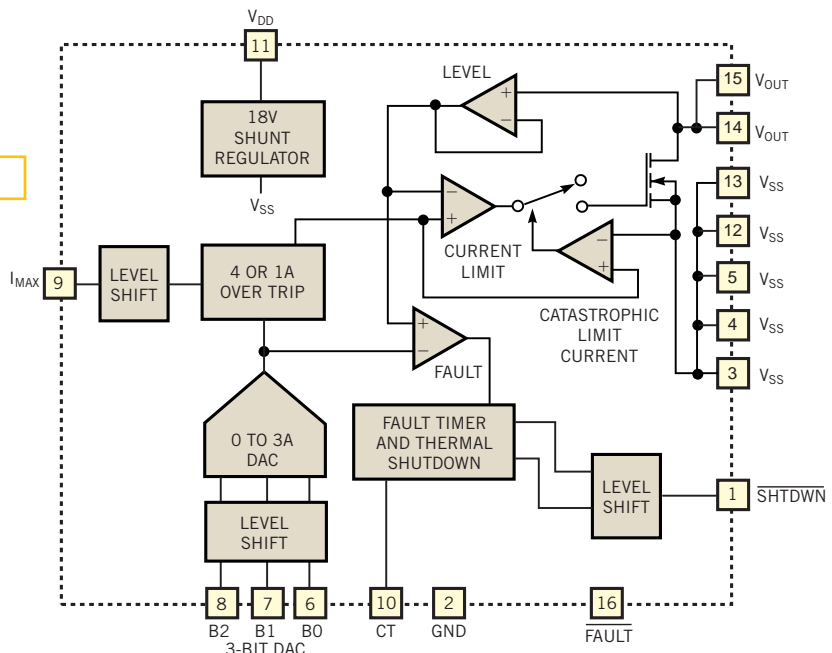

A 3-bit DAC in Unitrode's UCC3920 hot-swap manager allows you to program the fault-level trip current that suits your system.

programming resolution is 250 mA for currents of 0 to 500 mA, and 500 mA for currents of 500 mA to 3A. The UCC3920 handles -3 to -15V supply levels; its UCC3912 and 3915 siblings accommodate positive-voltage ranges of 3 to 8 and 7 to 15V, respectively. These managers incorporate a 4-bit DAC to allow fault-level programming of 0 to 3A with 250-mA resolution. The \$3.05 (1000) UCC3918 uses an external resistor rather than a DAC to provide linear fault-level programming of 0 to 4A.

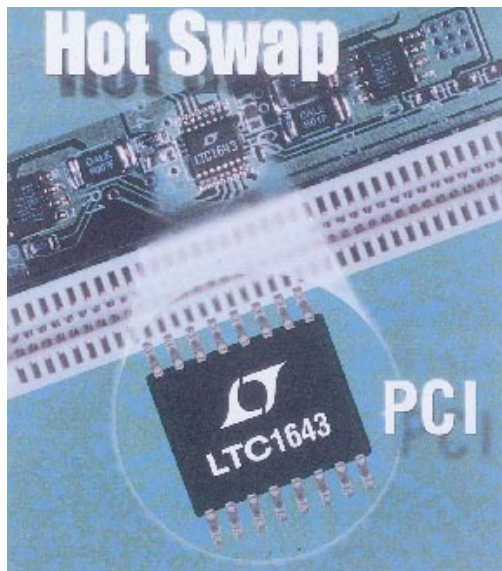The devices in **Table 1** that use external pass MOSFETs include charge-pump circuitry, which generates the gate voltages needed to turn on the n-channel MOSFETs. The ICs would be simpler and use less silicon if the external device were a p-channel MOSFET. However,



The LTC1643 hot-swap controller from Linear Technology makes live insertion/removal a safe operation in CompactPCI systems.

through a sad and immutable quirk of physics, a p-channel device uses about three times the silicon area of an n-channel MOSFET with the same ratings. It's more economical to connect a few capacitors and use an on-chip charge pump to drive an n-channel FET. **Table 1** gives no current ratings for the external-FET devices because that parameter is strictly a function of the MOSFET you specify.

**Figure 2** shows an elementary block diagram of a typical hot-swap IC that drives an external MOSFET. The charge-pump circuitry uses internal diodes and the external capacitors to configure a voltage tripler.  $V_{PUMP}$  provides plenty of head room to power the internal gate driver.  $I_{MAX}$ , the maximum sourcing current, is a programmable parameter. When the sensed output current is lower than fault level, the output MOSFET remains on. When the

## CURRENT SHARING ENHANCES PERFORMANCE AND FAULT TOLERANCE

Robert Pauplis, Senior Application Engineer, Vicor Corp

Power architects often employ multiple power supplies or power converters to increase output power or provide fault tolerance. You can usually increase power by paralleling two or more converters. Fault-tolerant systems also use power supplies in parallel, but they may use ORing diodes to isolate modules during an output fault.

Current sharing is a necessity when paralleling supplies to increase power. Although 2N-redundant supplies generally require no current sharing, current sharing improves system performance. N+1-redundant supplies require current sharing. Current sharing and how best to achieve it are important issues in managing multiple power supplies or power converters.

Current sharing brings a number of benefits to parallel arrays. It improves transient response because each of the N converters

shares the load step in a 1/N proportion. Each supply ages the same amount if equal current sharing exists, and thermal constraints are usually less demanding on systems using multiple supplies. Modular converters connected in parallel to increase power often find use in redundant applications, such as scalable power systems. The module array is readily expandable and may provide hot-swap capability.

You can implement current sharing in several ways; each method has advantages and disadvantages. Driver/booster arrays for the expansion of power usually contain one intelligent module or driver and one or more power-train-only modules or boosters. The driver sets and controls output voltage, and booster modules increase output power to meet system requirements. The advantages are that the array has only a single control loop,

and it provides excellent transient response because no loop-within-a-loop stability issues exist. An advantage of driver-booster arrays is that load sharing is accurate, even during dynamic load conditions. Driver-booster arrays using only one driver do not support redundant operation.

The "droop-share" approach to current sharing employs a resistance in series with the load or an active circuit that allows the output voltage to drop in response to increasing load. The droop-share circuit has the advantages of simplicity and low cost. However, it is limited in application because it usually requires manual adjustment of the output voltage to achieve current sharing. Also, the series resistance degrades output-voltage regulation in droop-share circuits.

DC-coupled, single-wire paralleling involves two or more identical modules, each containing a circuit

that monitors the current each supply delivers. This circuit actively adjusts the output voltage of each supply so that the multiple supplies deliver equal currents. However, this method has a number of disadvantages. Multiple control loops can cause stability problems, and they can provide poor transient response when a module fails. The method is also susceptible to single-point failures, which can defeat current sharing and, at worst, can cause a chain of failures.

A new fault-immune power architecture uses a digital current-sharing signal. Because it is an ac signal, dc blocking eliminates offsets in the system. Such modules allow designs to achieve high levels of availability and reliability. Additional advantages include excellent transient response, a high degree of immunity from system noise, and no loop-within-a-loop control problems.

current exceeds the fault level but is lower than the maximum sourcing current that  $I_{MAX}$  sets, the output remains on, and a fault timer begins to charge  $C_T$ . When  $C_T$  charges to a certain level, the output MOSFET turns off, and  $C_T$  slowly discharges. When  $C_T$  discharges to a certain low level, the hot-swap IC performs a retry, and the output MOSFET switches on again. The UCC3914 offers two distinct reset modes. In one mode, the IC repeatedly tries to reset itself if a fault occurs. In the other mode, when a fault occurs, the output stays off until you toggle a pin or until you turn the IC off then on again.

**FLOATING ON AIR**

Glancing at the 1000V-rated hot-swap ICs in **Table 1**, you might think that Unitrode uses an exotic process such as dielectric isolation to make its 1000V devices, but it does not. In a process called “bootstrapping” (derived from “pulling yourself up by your own bootstraps”), the \$1.54 (1000) UCC3917 floats at the supply voltage and uses charge-pump circuitry to generate its supply voltage. The negative-supply, \$1.40 (1000) UCC3913 and \$1.42 (1000) UCC3921 use the negative input voltage as reference and derive their power from an external resistor connected to ground. The 1000V limit for these ICs is not etched in stone; the maximum voltage is a function of the ratings of the external components.


Designed for RAID systems, Harris Semiconductor’s HIP1012 dual-voltage

hot-swap controller safely applies and removes power to and from a disk drive, allowing you to swap drives during service operations. The IC provides active current limiting for your pin-selectable choice of dual-supply power buses: 5 and 12V or 5 and 3.3V. In a typical application diagram, the two current-sensing resistors,  $R_{SENSE}$ , provide inputs for the IC’s overcurrent-protection circuitry (**Figure 3**). When the current through either resistor exceeds the user-programmed value, the controller en-

ters its current-regulation mode, and the time-out capacitor,  $C_{TIM}$ , starts charging. When  $C_{TIM}$  charges to a 2V threshold, the IC switches off the n-channel MOSFETs.

The time-out period ranges, for example, from 4.4 msec with  $C_{TIM}=22$  nF to 20 msec for  $C_{TIM}=100$  nF. If a fault is three times the current-limit level, the controller turns off the MOSFETs in less than 3  $\mu$ sec before entering its time-out period. The turn-off time is less than 1  $\mu$ sec for a dead short. A rising edge on either power-on pin

**Figure 2**

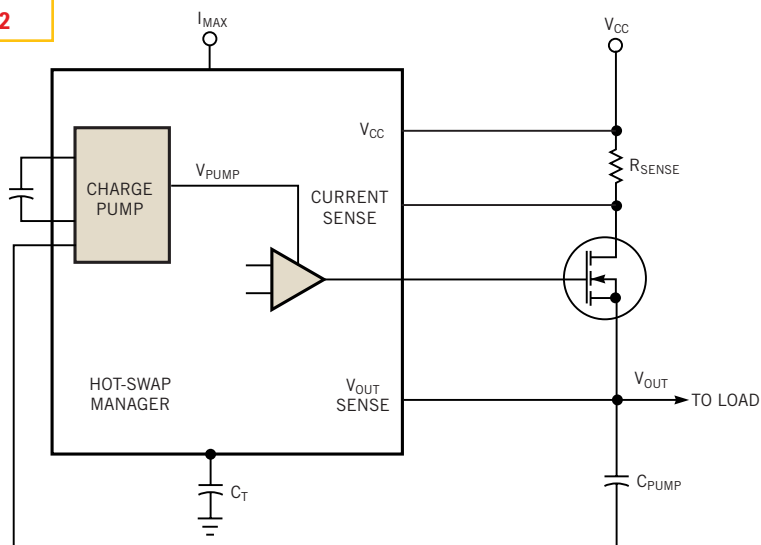

Bootstrapping via  $C_{PUMP}$ , an on-chip charge-pump circuit, provides the gate drive for the external MOSFET used with most hot-swap controllers.

**FOR MORE INFORMATION...**

For free information on power-management ICs such as those described in this article, circle the appropriate numbers on the postage-paid Information Retrieval Service card or use *EDN's* InfoAccess service. When you contact any of the following manufacturers directly, please let them know you read about their products in *EDN*.

**Harris Semiconductor**

Melbourne, FL  
1-407-729-5973  
fax 1-407-729-5321  
www.semi.harris.com  
Circle No. 326

**Linear Technology Corp**

Milpitas, CA  
1-408-432-1900 ext 2453  
fax 1-408-434-6441  
www.linear-tech.com  
Circle No. 327

**Texas Instruments Inc**

Dallas, TX  
1-800-477-8924 ext 4500  
www.ti.com/sc/power  
Circle No. 328

**Unitrode Corp**

Merrimack, NH  
1-603-424-2410  
fax 1-603-424-3460  
www.unitrode.com  
Circle No. 329

**Vishay Siliconix**

Santa Clara, CA  
1-408-988-8000  
fax 1-408-567-8950  
www.siliconix.com  
Circle No. 330

**SUPER CIRCLE NUMBER**

For more information on the products available from all of the vendors listed in this box, circle one number on the reader service card. Circle No. 331


resets the controller. For power-up control of supply sequencing, you can program the two MOSFETs' turn-on ramps by selecting suitable values for  $C_{GATE}$ .

$R_{GATE}$  is a 10 to 200 $\Omega$  resistor that prevents current oscillation. As usual, an internal charge pump provides gate drive (17.4V for a 12V bus, 11.4V for 3.3 or 5V) for the MOSFETs.  $V_{DD}$  is the 12V supply for the controller. You use the optional decoupling filter if the 12V chip supply also powers the load; if you use a dedicated chip supply, the network may be unnecessary. The HIP1012 costs \$4.85 (1000). Harris offers evaluation boards for both general-purpose and RAID applications.

Apropos of multiple supplies, Linear Technology's LTC1643 controls hot-swap operations for four power rails: -12, 3.3, 5, and 12V (Figure 4). Intended for PCI-bus (CompactPCI) applications, the IC provides on-chip switches for the -12 and 12V rails and controls external n-channel MOSFETs for the 3.3 and 5V rails.  $R_1$  and  $R_2$  provide current-fault detection;  $R_7$  and  $C_1$  provide current control-loop compensation. After the external pass transistors turn on, the current in each transistor increases until it reaches its current limit. Each supply then powers up at the rate  $dV/dt=50 \mu A/C_1$ , or at a rate determined by the current limit and the load capacitance, whichever is slower. The IC ignores current-limit faults when the timer pin ramps up toward 0.9V less than the 12V input level.


The LTC1643 features fold-back current limiting. The low-value current-sensing resistors in series with the external MOSFETs set the current limits for these supplies. For a 0.005 $\Omega$  resistor in the 3.3 or 5V line, the current limit is 10.6A, folding back to 1.5A for a short

Figure 3

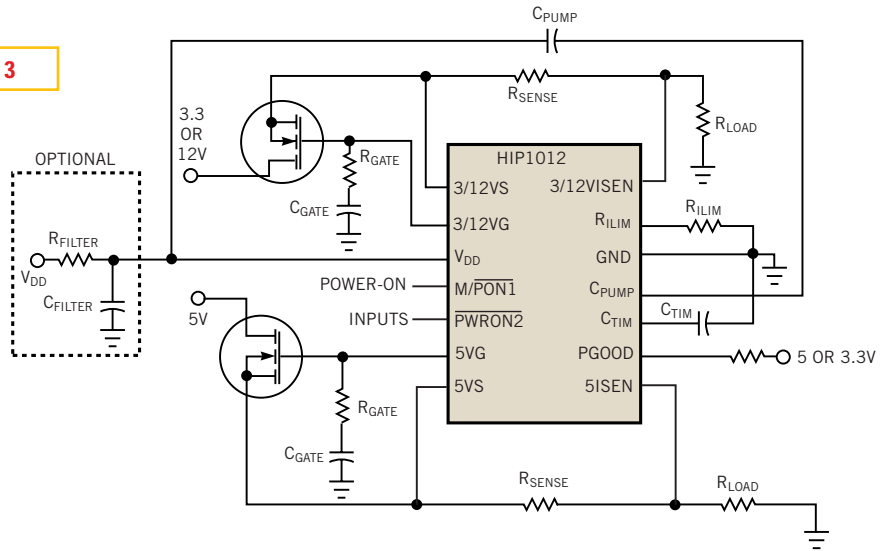


Live insertion/removal is a must in RAID systems; the HIP1012 from Harris Semiconductor provides hot-swap protection for the disk-drive power buses in these redundant systems.

Figure 4

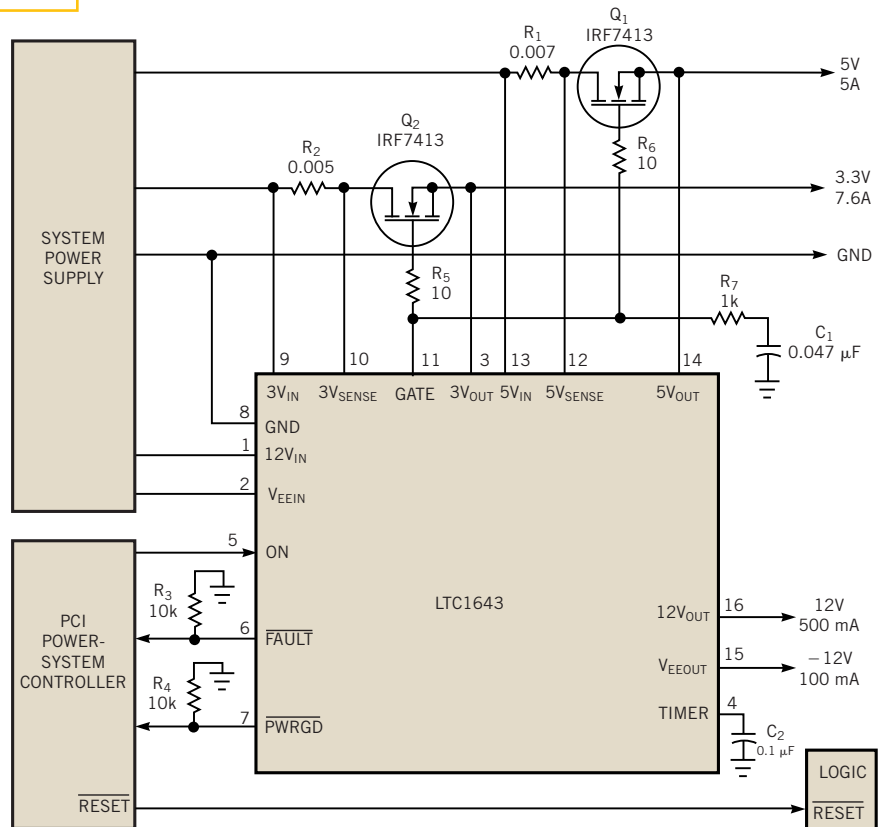

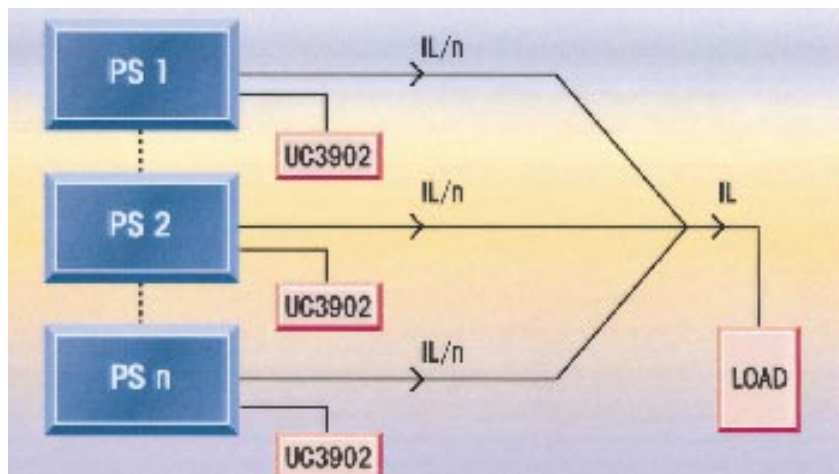PCI applications can use as many as four power buses; Linear Technology's LTC1643 provides hot-swap protection for all four buses.





A handful of UC3902 load-share ICs from Unitrode can prevent multiple supplies from oversupplying or undersupplying their share of load current.

LTC1643 costs \$4.25 (1000) and comes in two versions: The LTC1643H targets PCI applications that control hot swapping on the motherboard; the LTC1643 controls hot swapping on the PCI card. **Reference 2** gives a wealth of application information for the LTC1643.

Texas Instruments calls its hot-swap controllers “power-interface switches.” The \$1.65 (2000) TPS2211 single-slot switch for a PC (PCMCIA) Card has 90-m $\Omega$  switches for the 3.3 and 5V power supplies. Break-before-make operation provides hot-swap capability. The \$3.22 (2000) TPS2206 provides similar capabilities for controlling two PC Cards. Its three-lead serial interface is compatible with CardBus controllers. The \$3.02 (2000) TPS2205 two-slot controller is similar to the TPS2206, but it uses an interface that is compatible with IC-based PC Card controllers available from myriad manufacturers. Finally, TI’s 88-cent (2500) TPS2014 and 88-cent (2500) TPS2015 USB hub controllers provide 95m $\Omega$  MOSFET switches with controlled rise and fall times that protect USB systems from hot-swap and transient damage.

#### SHARE AND SHARE ALIKE

It is often beneficial to connect multiple power supplies in parallel to increase total power capacity, achieve redundancy, or both. **Reference 3** discusses some of the issues involved in configuring redundant multiple-supply systems. For various reasons, it is important that all the supplies share the load current as equally as possi-

ble. The sidebar “Current sharing and fault tolerance,” describes several current-sharing schemes. Most power-supply manufacturers offering products for parallel connection build the current-sharing mechanisms into the supplies, often with hot-swapping capability. If you wish to configure your own multiple-supply systems, several load-sharing ICs offer an easy and efficient way to optimize load sharing among the supplies.

The UC3902 from Unitrode Corp is an eight-pin device that balances the current drawn from independent, parallel-connected power supplies. It effects load sharing by adjusting each supply’s output current to a level that is proportional to the voltage on a shared bus. **Figure 5** shows two UC3902s connected to their respective supplies in a multiple-supply system. The master supply, designated as the supply that regulates to the highest voltage, drives the share bus with a voltage that is proportional to its output current. The UC3902 trims the output voltage of the other paralleled supplies so that each supply supports its share of the load current. The currents need not necessarily be equal. By appropriately scaling the current-sense resistor  $R_{SENSE}$ , you can connect supplies with different output-current capabilities so that each supply provides the same percentage of its output-current capability for a given load.

The UC3902 is compatible with power supplies that incorporate remote output-voltage sensing. The IC trims the supply’s output by injecting a small current into the

output-voltage sense line. The differential share bus maximizes noise immunity and accommodates voltage drops in each power supply's ground-return line. **Reference 4** and the UC3902 data sheet detail how to determine the component values in **Figure 5**. The UC3902 costs \$1.62 (1000). An older sibling of Unitrode's UC3902, the UC3907, comes in a 16-pin DIP or SOIC, or a 20-pin PLCC and offers optocoupler-driving capability.

Vishay Siliconix takes a different approach to current sharing with its Si9143CG buck-controller IC. This synchronous controller targets point-of-use dc/dc conversion in servers and desktop computers in which shared supplies can reduce stress on power-supply components and thereby increase system reliability. The IC ensures equal current sharing by connecting the PWM and sync pins to make multiple controllers' duty cycles identical. The sync pin forces all the controllers to simultaneously start their duty cycles; the PWM

pin forces the controllers to simultaneously finish their duty cycles. Thus, all controllers run at the same frequency and phase; they can also run from the same power bus and deliver power to the same output bus. Operating as fast as 1 MHz, the Si9143CG ensures equal current sharing to within 1%. The device costs \$1.80 (25,000).

Issues such as ease of use, service accessibility, and reliability make both hot swapping and current sharing important considerations in system design. ICs that painlessly help you realize these functions make it possible for you to ignore these power-supply issues and devote your efforts to more productive tasks. □



#### References

1. Nelson, Todd, "Design solutions for hot swap control," Linear Technology Corp, 1998.
2. Reay, Robert, "Hot swapping the PCI bus using the LTC1643," Linear Technology, 1998.

3. Travis, Bill, "Onboard regulators," *EDN*, February 16, 1995, pg 34.
4. Balogh, Laszlo, "The UC3902 load-share controller and its performance in distributed power systems," Application Note U-163, Unitrode Corp.

**IN THE NEXT ISSUE OF EDN**  
.....  
**Our December 5 issue provides details of the Top 100 products of the year. And check out the expanded Tech Toys section—just in time for the holidays.**