



Figure 3

One dual op amp and a handful of components turn a LED into a dual-purpose device.