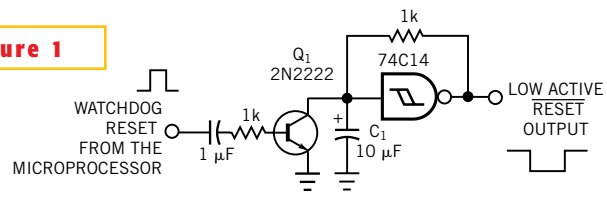


**Figure 1**



**This watchdog circuit uses ac triggering to avoid watchdog-signal hang-up problems.**