



**Figure 4**

A switch with hysteresis and a few passive elements produce an RC oscillator.