



**Figure 1**

**A current-sensing circuit derives its power from the 4- to 20-mA current loop.**