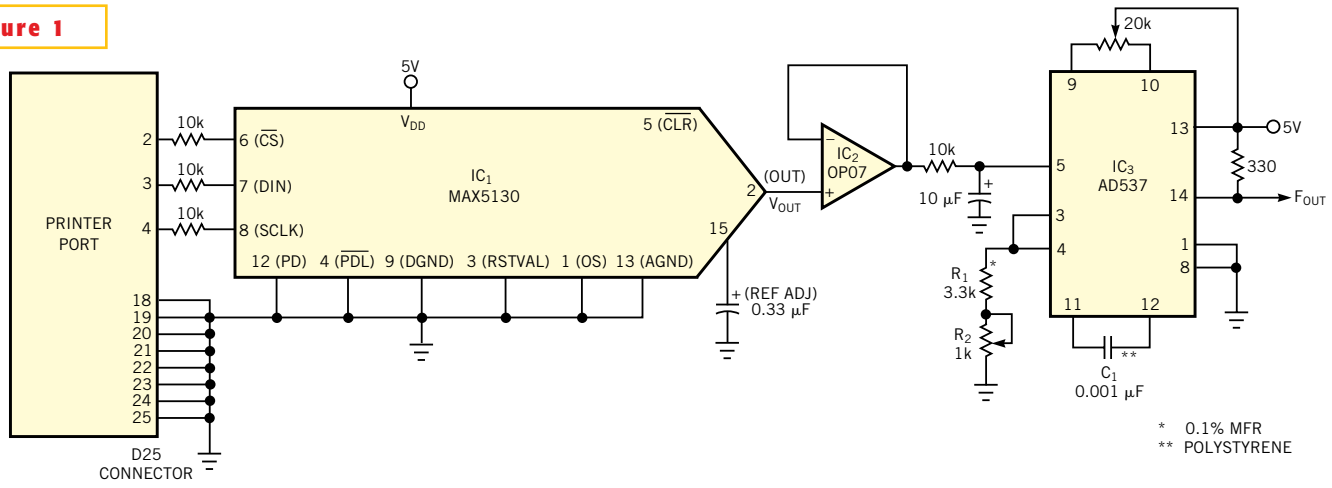


Figure 1



Turn your PC's printer port into a programmable frequency generator with this simple circuit.