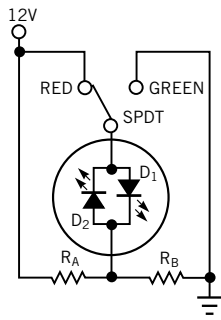


**Figure 1**



**This switching circuit wastes power and does not work with low supply voltages.**