



Figure 1

The buck-converter topology uses two n-channel MOSFETs. Q_1 is the switching or control MOSFET, and Q_2 is the synchronous rectifier. L and C comprise the output filter, and R_L is the load resistance.