



Figure 2

This circuit provides safe power-up and power-down sequencing for sensitive GaAs FETs and MMICs.