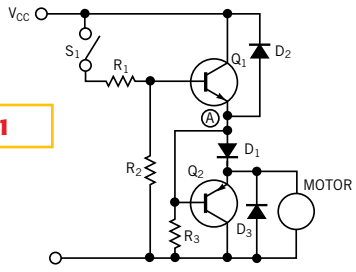


Figure 1



This circuit provides both motor-drive and braking functions.