



Figure 1

For ultrasound applications, a single, low-noise reference circuit can drive as many as 1000 ADCs.