



**Figure 2**

For ultrasound applications, a precision, low-noise reference circuit can drive as many as 32 ADCs.