



Figure 3

(b)

A test circuit configures the 555 timer as a voltage-controlled oscillator so that the control-voltage input determines the output frequency (a). The simulation results show the control-voltage input and the resulting threshold voltage in the top plot and the change in output frequency in the bottom plot