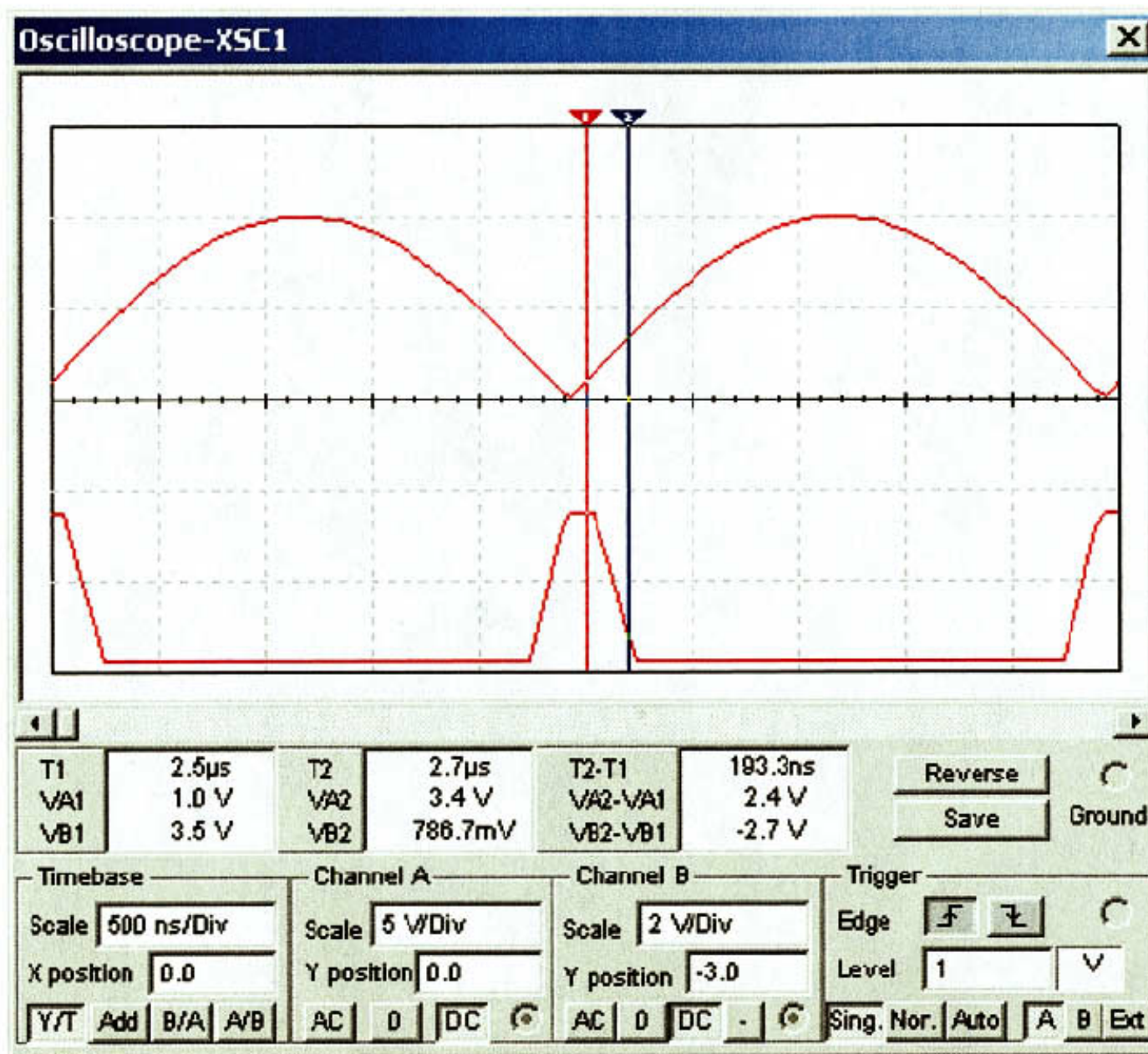


Figure 3



Channel A is the rectified (absolute-value) output of IC_{1B}; Channel B is the output of the comparator.