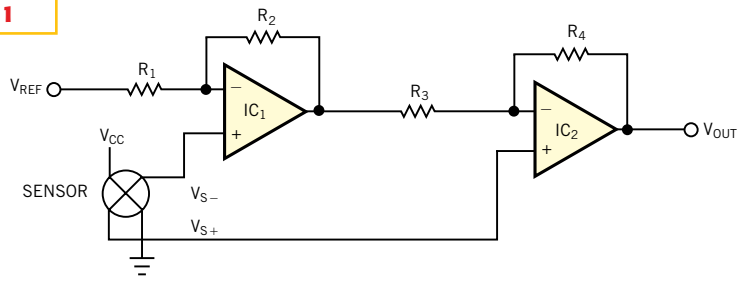


**Figure 1**



**This circuit is a good sensor amplifier but suffers from a lack of variability.**