



**Figure 1**

This circuit sets audio gain logarithmically in 3-dB steps.