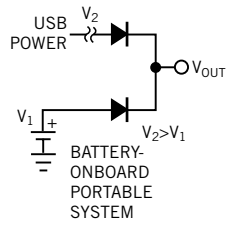


Figure 1



A diode-OR connection is effective but lossy.