



Figure 1

This classic buck regulator suffers from excessive negative phase-node voltage.