



Figure 1

The op-amp feedback keeps the phototransistor's current constant, so the circuit requires no adjustments for transfer gain.