



Figure 1

You can eschew expensive dc/dc converters by using this inexpensive circuit to drive a white LED from a single battery cell.