



Figure 1

This circuit can both boost and step down the output voltage, depending on whether the input voltage is lower or higher than the output voltage.