



**Figure 1**

This ARINC 429 transmitter operates from a single 5V supply and meets all timing requirements of the 429 spec.