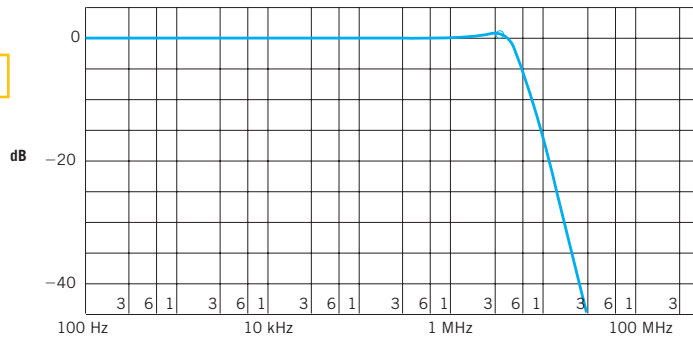


**Figure 2**



The typical filter response for the circuit of Figure 1 is  $R_1 + R_2 = 332\Omega$ .