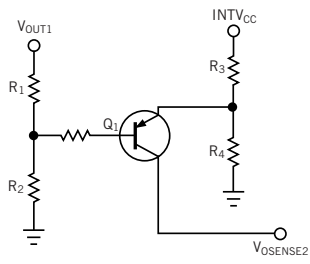


Figure 1



A simple one-transistor circuit synchronizes two outputs.