



Figure 2

You can obtain multiple-output sequencing by adding ORing diodes.