



Figure A A floating, battery-powered laser simulator sets the desired junction drop across the output terminals. Amplifier feedback controls Q_2 's V_{CE} according to the potentiometer voltage.