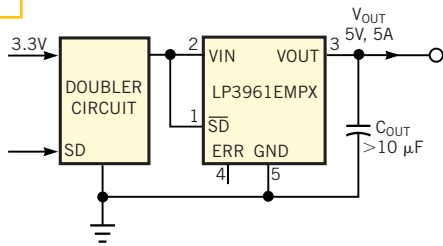


Figure 3



You can tighten voltage-regulation specs in Figure 1's circuit by adding a linear regulator.