



Figure 1

The 741 illustrates how an op amp works and demonstrates many shortcomings of general-purpose devices in low-voltage applications.