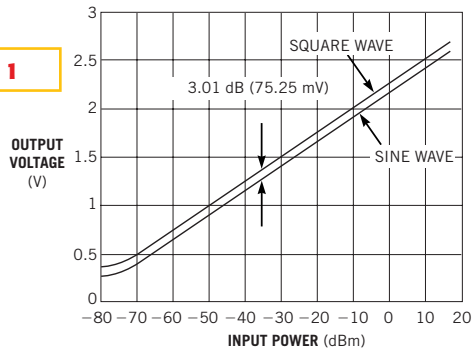


Figure 1



This circuit provides an output voltage that is linearly proportional to the input power in watts.