



Figure 1

This small, simple circuit produces 5V at 5 mA from a -48V input.