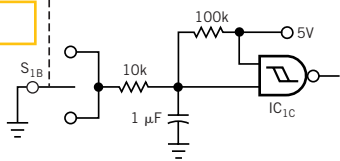


Figure 3



You can simplify the oscillator-enable structure, as shown.