



Figure 2

This Colpitts oscillator uses a current-feedback amplifier to provide a clean sinusoidal output.