



Figure 1

In this LED-driver circuit, a switching converter, IC₁, and associated components lets you mix LED quantities and types.