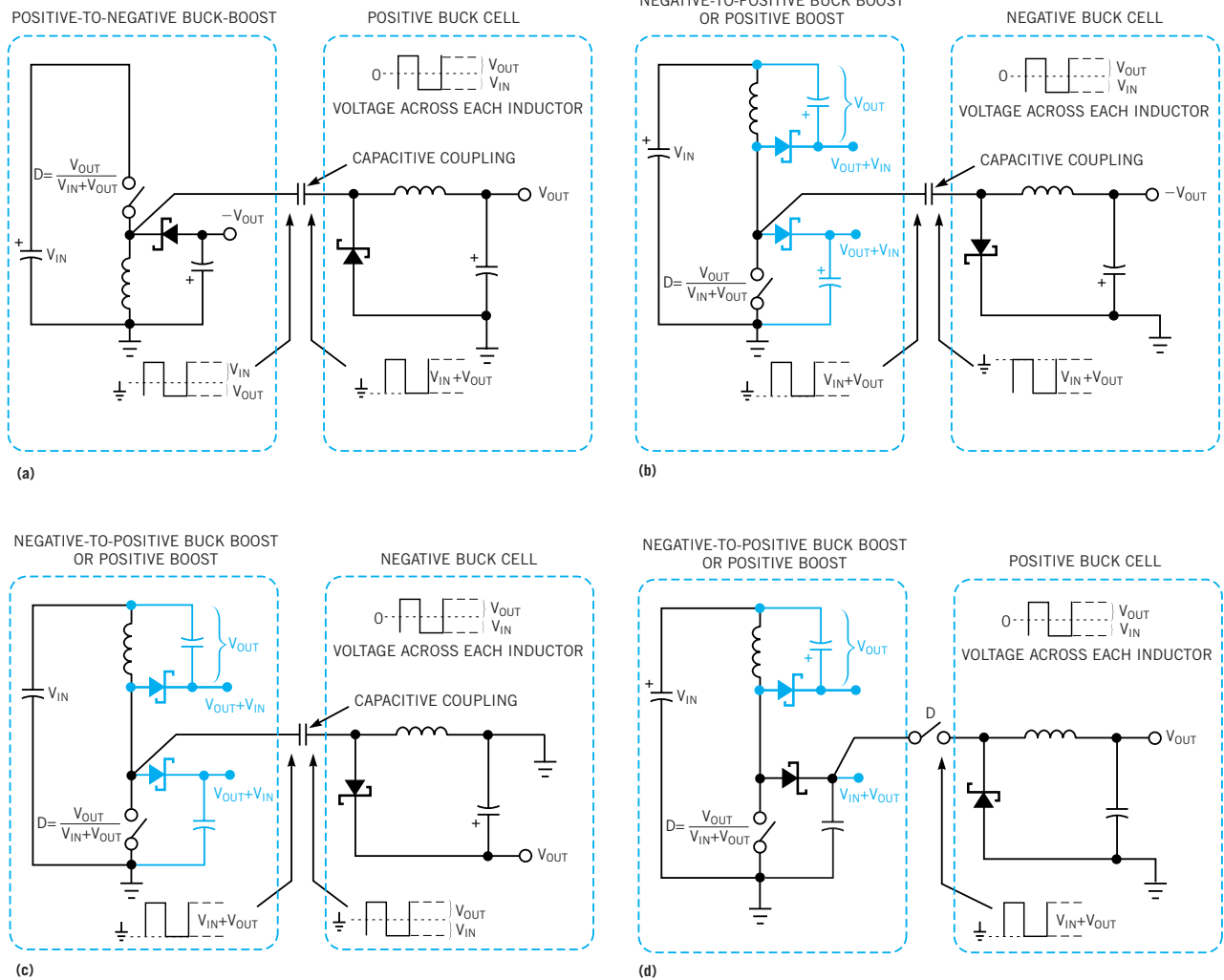


**Figure 1**



Examples of combined dc/dc converter topologies are the zeta (a), Cuk (b), sepic (c), and boost-buck cascade (d).