



Figure 2

A zener diode provides fixed gate drive to the MOSFET when the input voltage varies significantly.