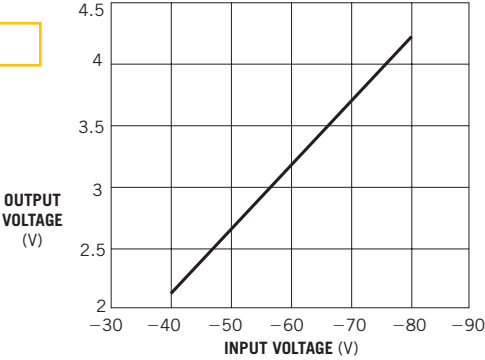


**Figure 2**



The circuit in Figure 1b produces an output that's a linear function of the negative supply voltage.