



**Figure 3**

**This circuit controls the I/O and core-voltage power-on and power-off sequencing.**