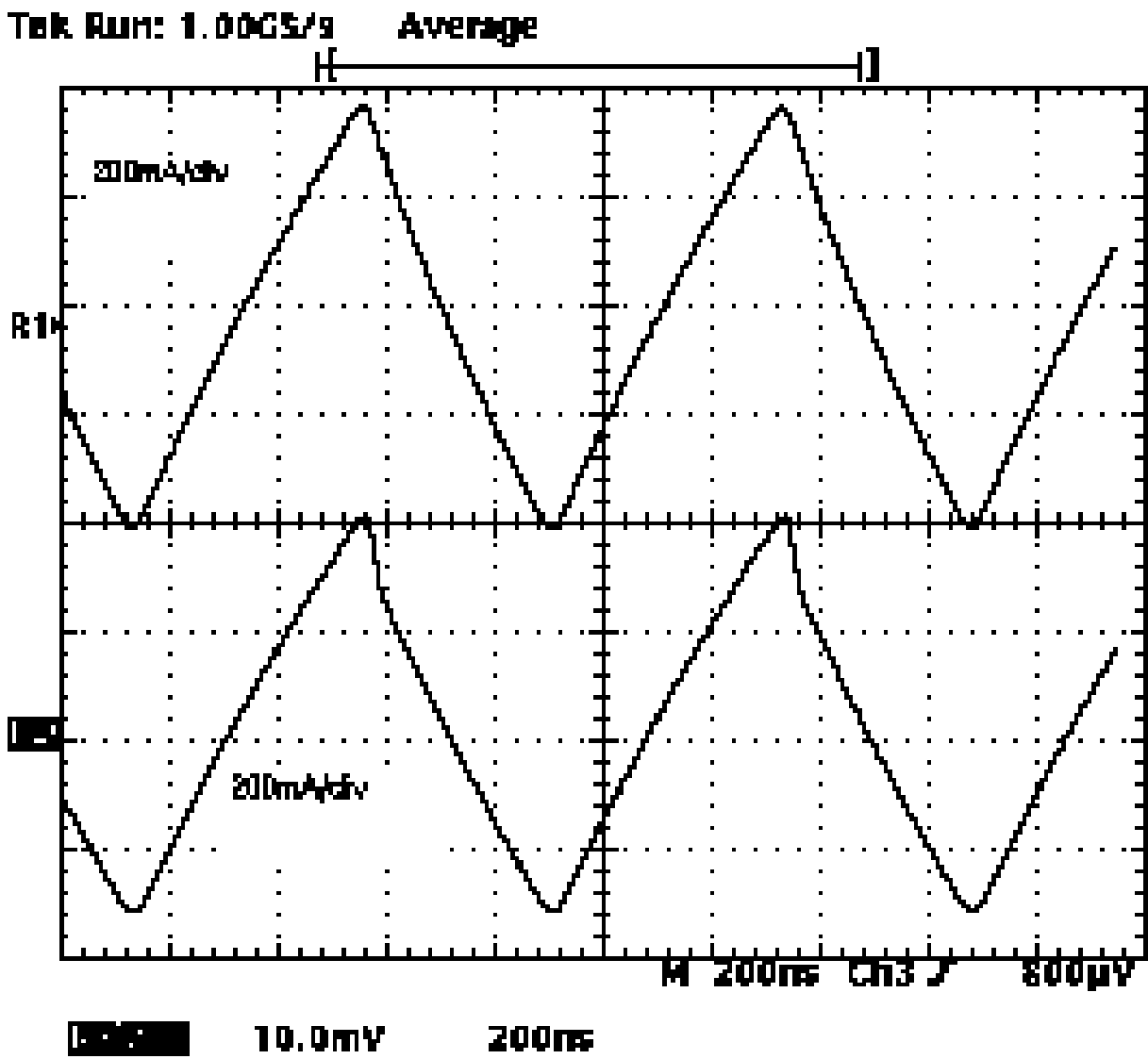


Figure 3



In the circuit in Figure 1, the output capacitor's peak-to-peak current ripple is equal to the inductor's peak-to-peak ripple with 1A output.