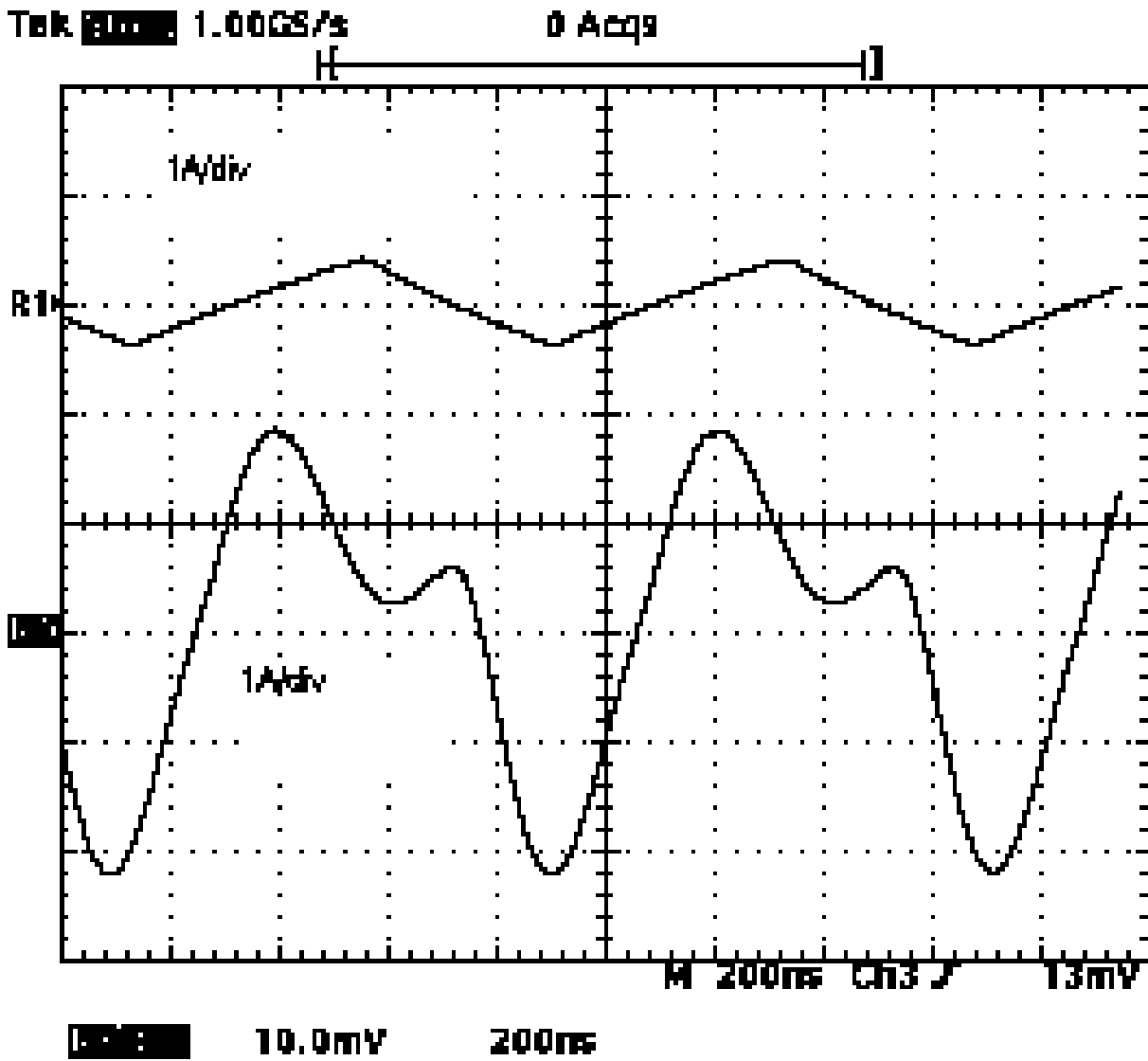


Figure 4



In the circuit in Figure 2, the output capacitor's peak-to-peak current ripple is five times as high as the inductor's peak-to-peak ripple and, therefore, five times as high as the current ripple shown in Figure 3 with 1A output.