



The JFET in this circuit effectively multiplies the value of  $R_1$ .