



Figure 3

An operational amplifier provides yet another means to achieve high impedance for capacitive sensors.