



Figure 1

Similar to a bridged audio amplifier, this op-amp circuit delivers output-voltage swings to the load beyond the span of the power supplies.