



Figure 3

A bidirectional level shifter translates data and clock signals from positive levels to negative levels, and vice versa.