



**Figure 1**

A standard redundant configuration of power-supply modules uses ORing diodes at the outputs.