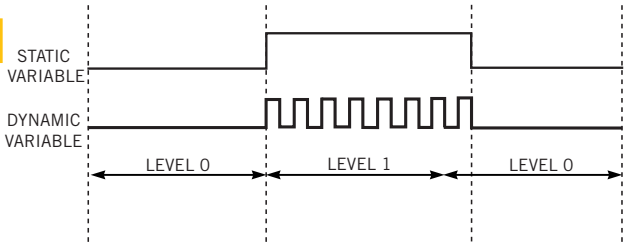


Figure 1



You can improve the reliability of an electronic-control output by using an oscillating, instead of steady-state, signal to represent a logic-high state.